

Computer Organization, Spring 2022

LAB 4 : Single-Cycle CPU


Due : 2022/5/11 23:59

1. Goal

- To realize how to set the control signal in different instruction type.(Decoder & ALU Controller)
- To clarify how sign-extend work.
- Connect all datapath to form a single cycle CPU

2. HW Requirement

-

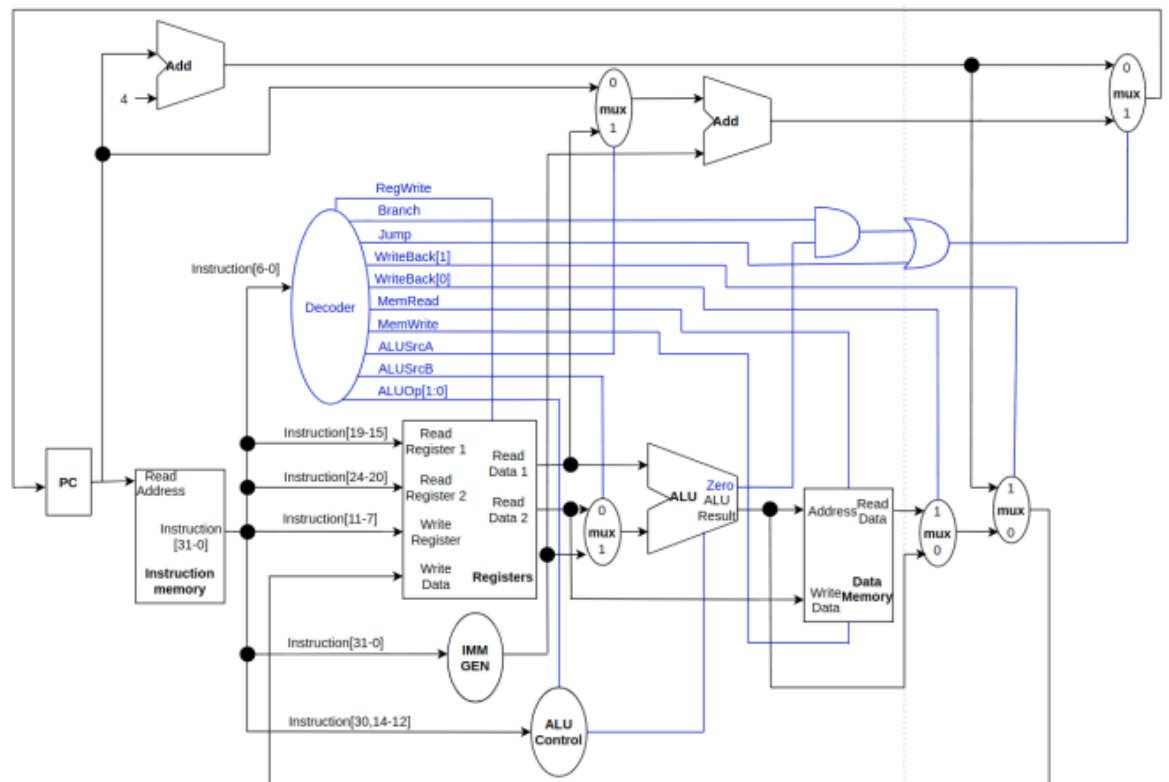

- **Implement bellow instruction for testing data(70%)**
 - **add**
 - **slt**
 - **addi**
 - **lw**
 - **sw**
 - **jal**
 - **jalr**
 - **You world not get any score for this part if you
program can't pass the test by script.**
- **Experiment(30%)**
 - **What's the problem you encounter?(5%)**
 - **Your implement detail.(20%)**
 - **Anything you want to say.(5%)**

3. Hand in

- **\$(groupN)_\$(studentid1)_\$(studentid2).zip**
 - **\$(groupN)_\$(studentid1)_\$(studentid2)**
 - **\$(studentid1)_report.pdf**
 - **\$(studentid2)_report.pdf**

■ {*.v}

```
group99_0811111_0811999/  
├── 0811111_report.pdf  
├── 0811999_report.pdf  
├── Adder.v  
├── ALU_Ctrl.v  
├── alu.v  
├── answer.txt  
├── Data_Memory.v  
├── Decoder.v  
├── demo.sh  
├── Imm_Gen.v  
├── Instr_Memory.v  
├── Instruction.txt  
├── Makefile  
├── MUX_2to1.v  
├── ProgramCounter.v  
├── Reg_File.v  
├── Simple_Single_CPU.v  
└── testbench.v
```

- Your report should be in PDF format.
- Report
 - Experiment

4. Grade

- Pass the script testing. 70%
- Experiment. 30%

5. Q&A

- Feel free to ask on HackMD if you need.
 - [Lab4 討論區](#)
- We will not debug for you

6. Reference

- [RISC V\(https://riscv.org/technical/specifications/\)](https://riscv.org/technical/specifications/)